
Drops of LTSpice

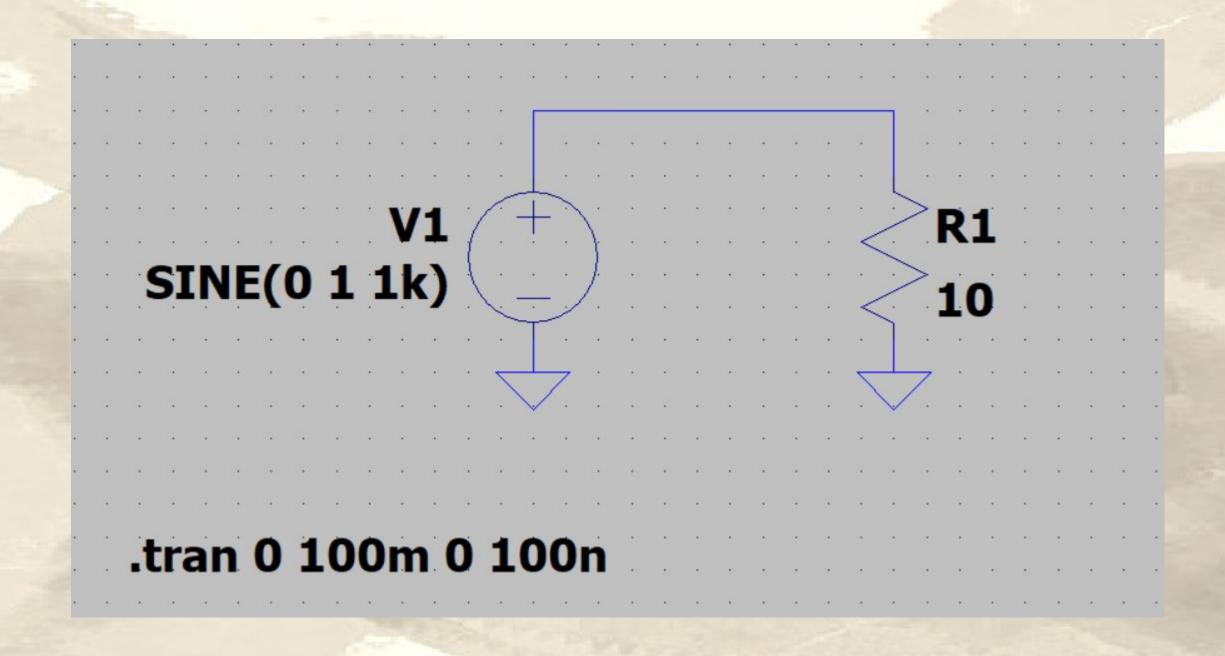


Using arbitrary current sources as Loads

Everyone has done something like this...




It is a voltage source and a load. It could not be simpler.

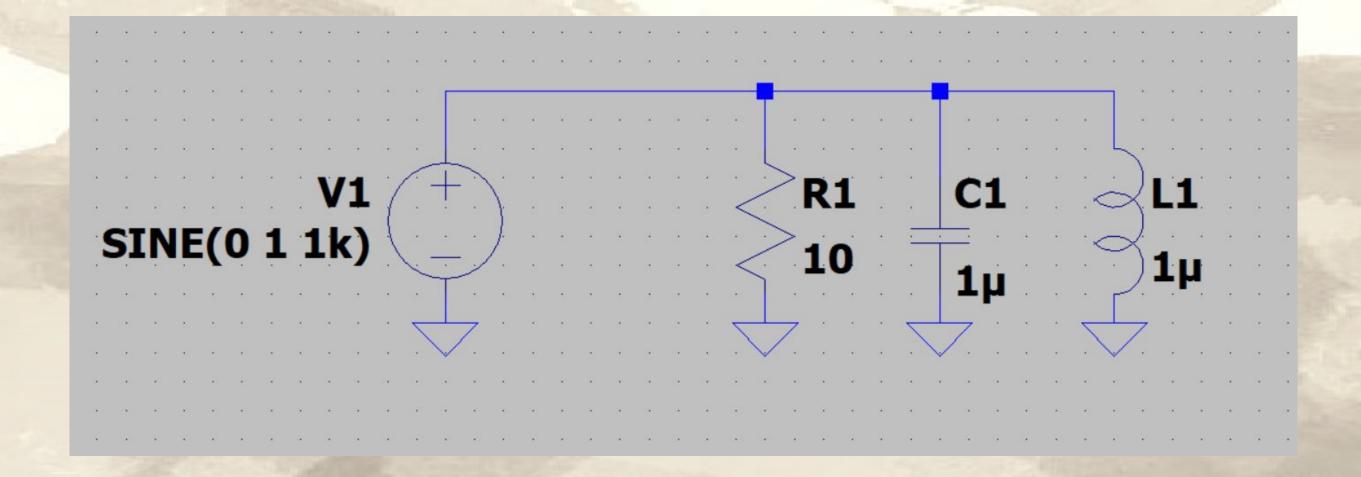But... what about when we need more complex loads?




Can we simplify this?

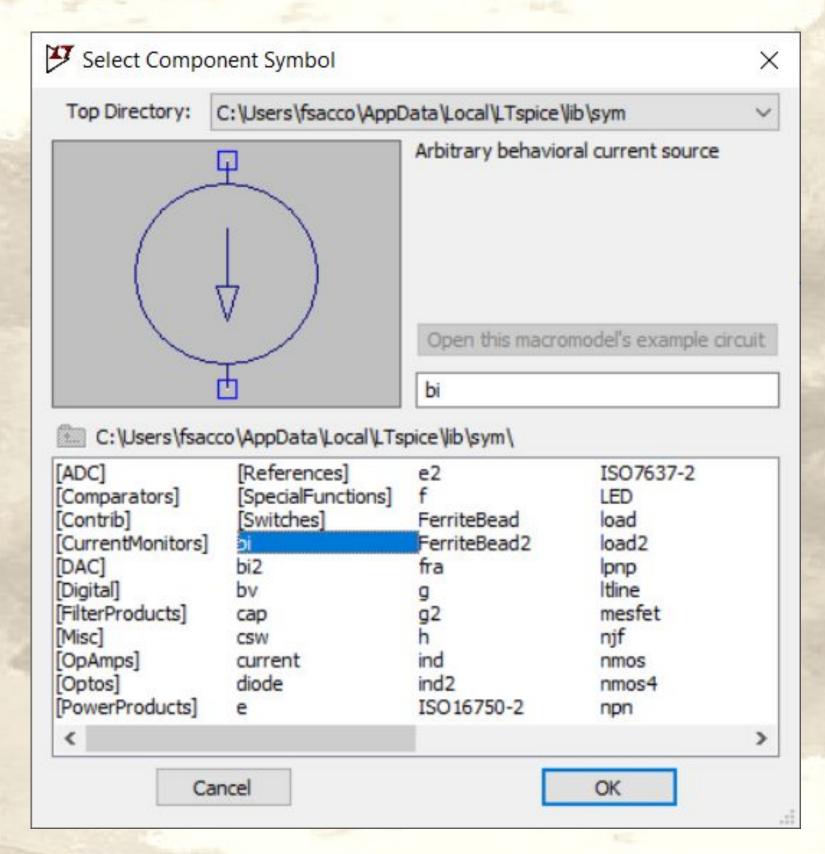Yes! Using the Arbitrary Behavioral Current Source.




It is possible to implement a chain based on a mathematical function.

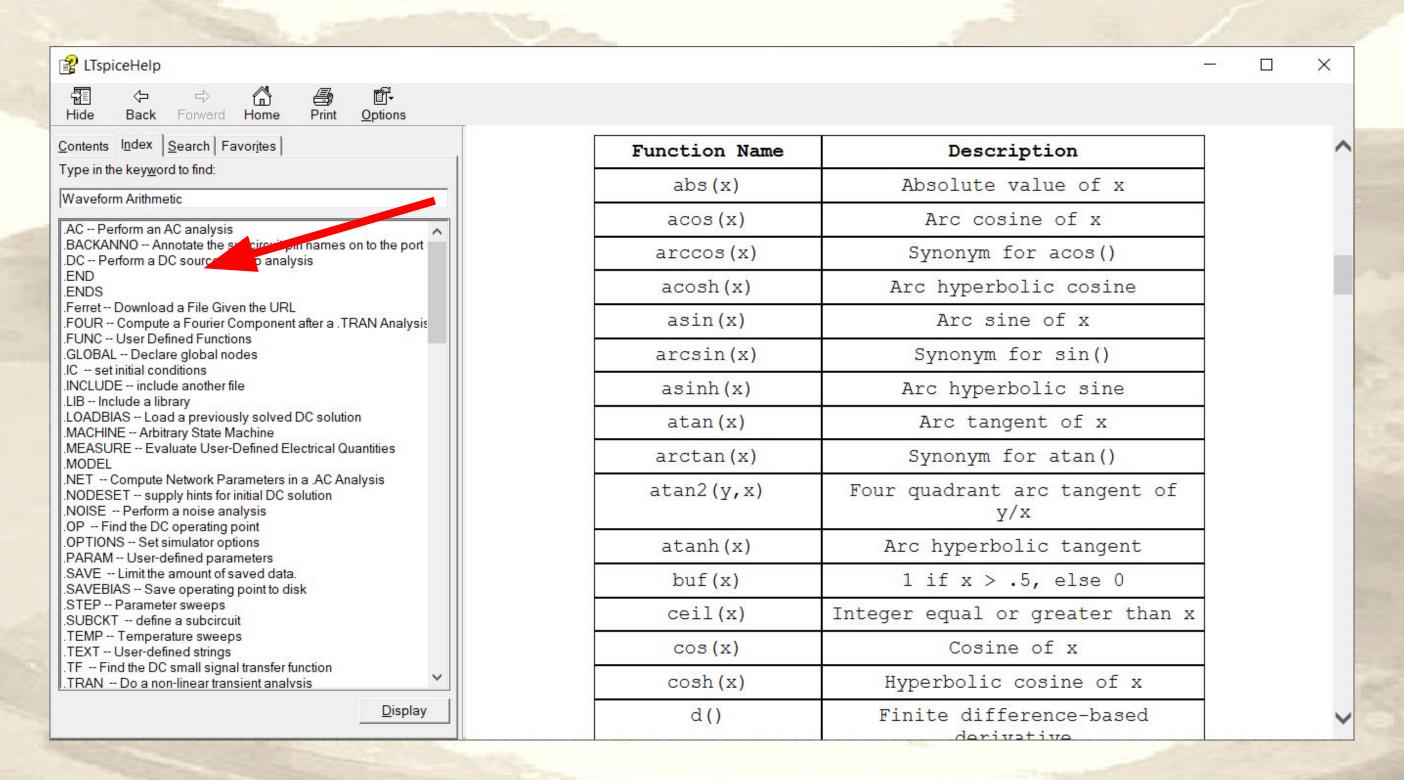And this component respects the same mathematical functions that we saw previously.



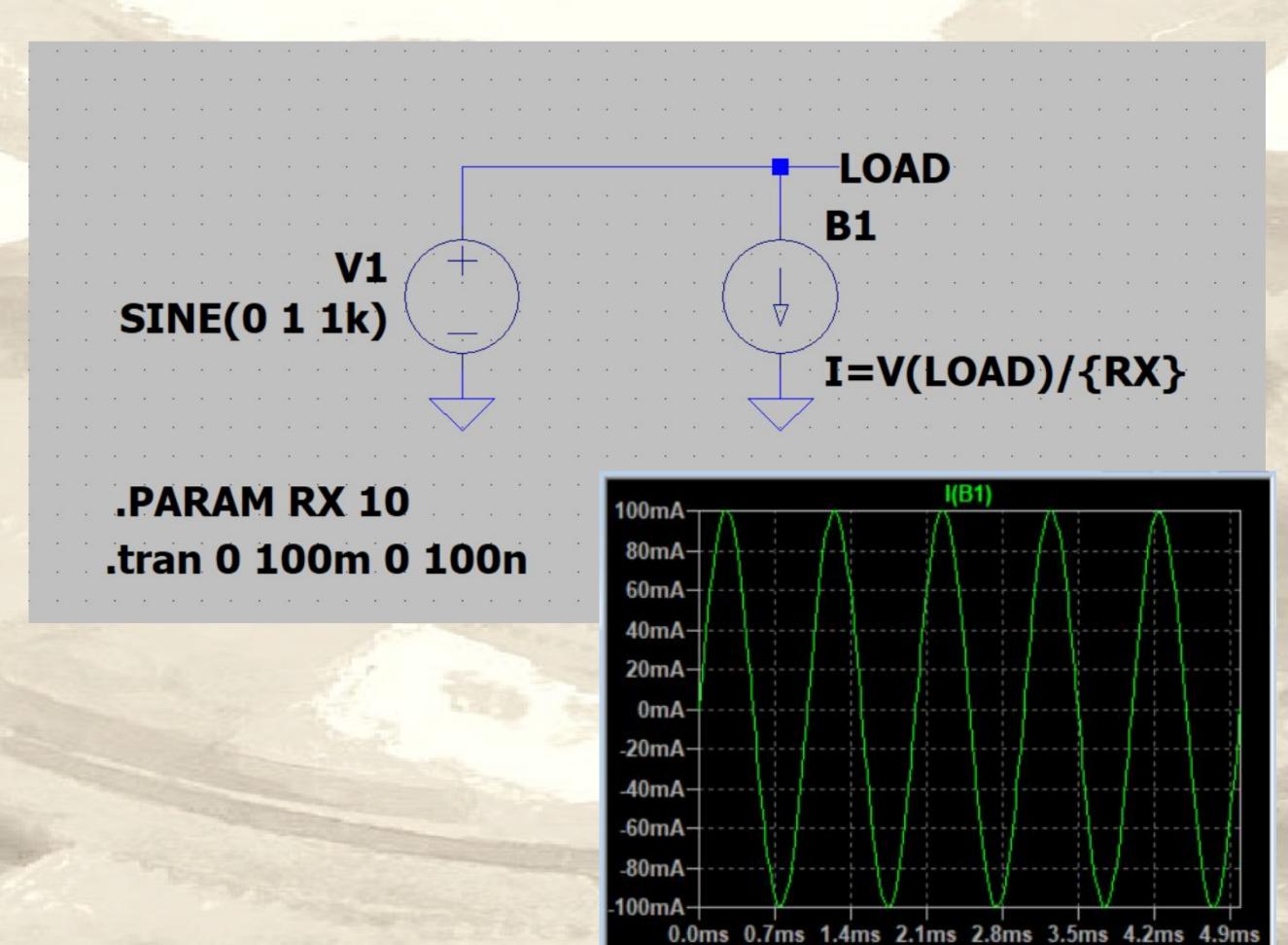
For example... once we know that I=V/R, it is easy to create a resistive load.




The current over a capacitor is:

$$i(t) = C \frac{\mathrm{d}v(t)}{\mathrm{d}t}$$

The math function ddt() can do this job.

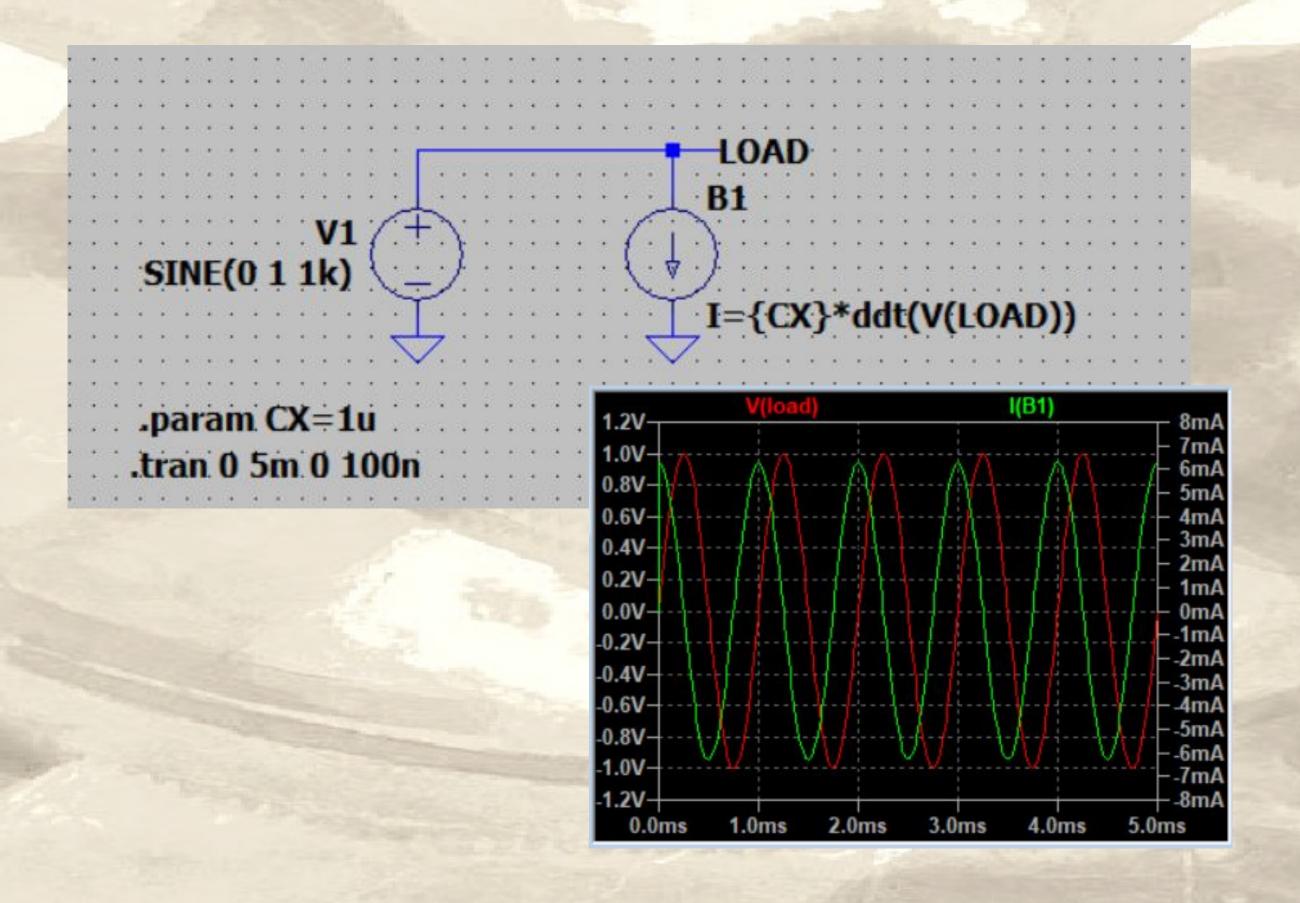


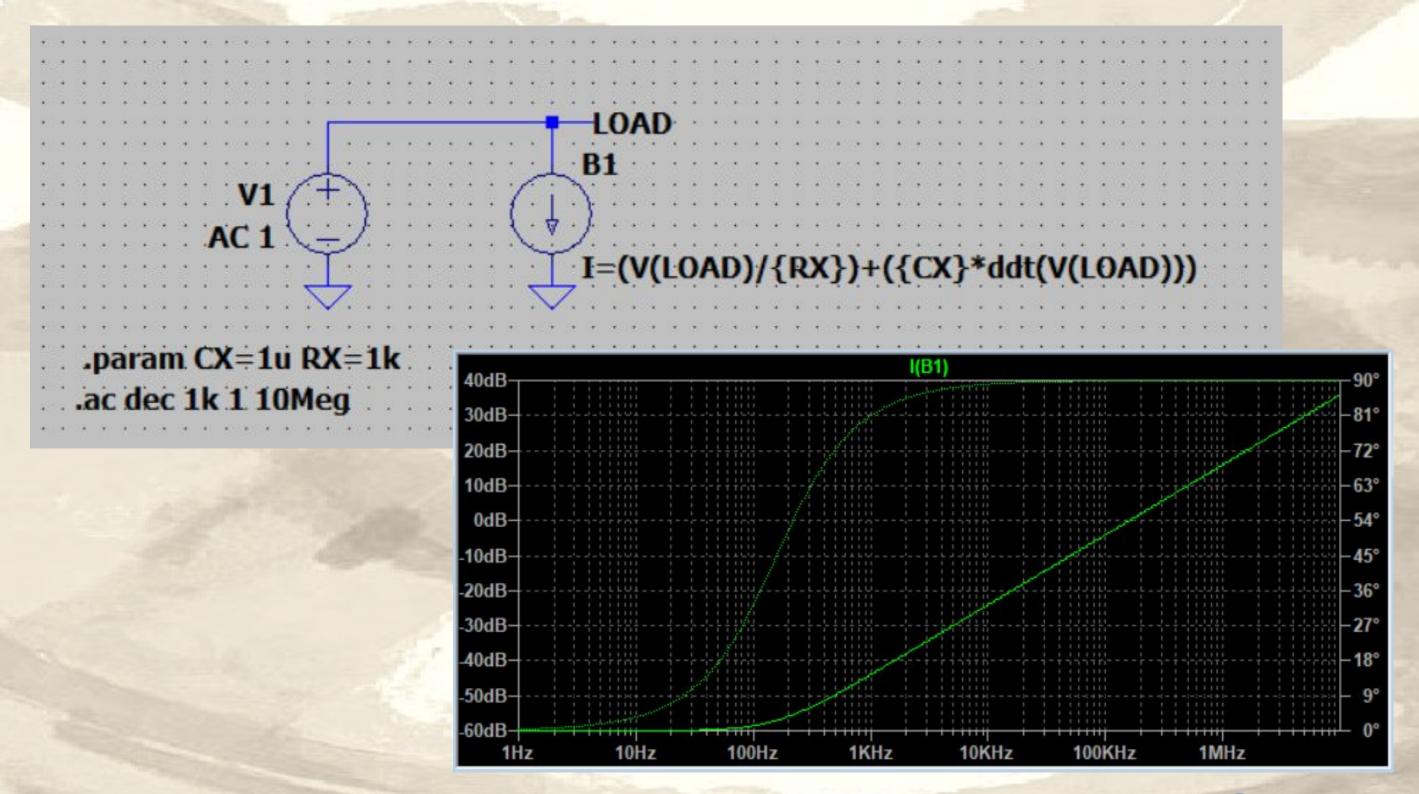A composition of fillers can be made. Here we have a resistive load in series with a capacitive one.



It is even possible run an AC analysis on loads like this.

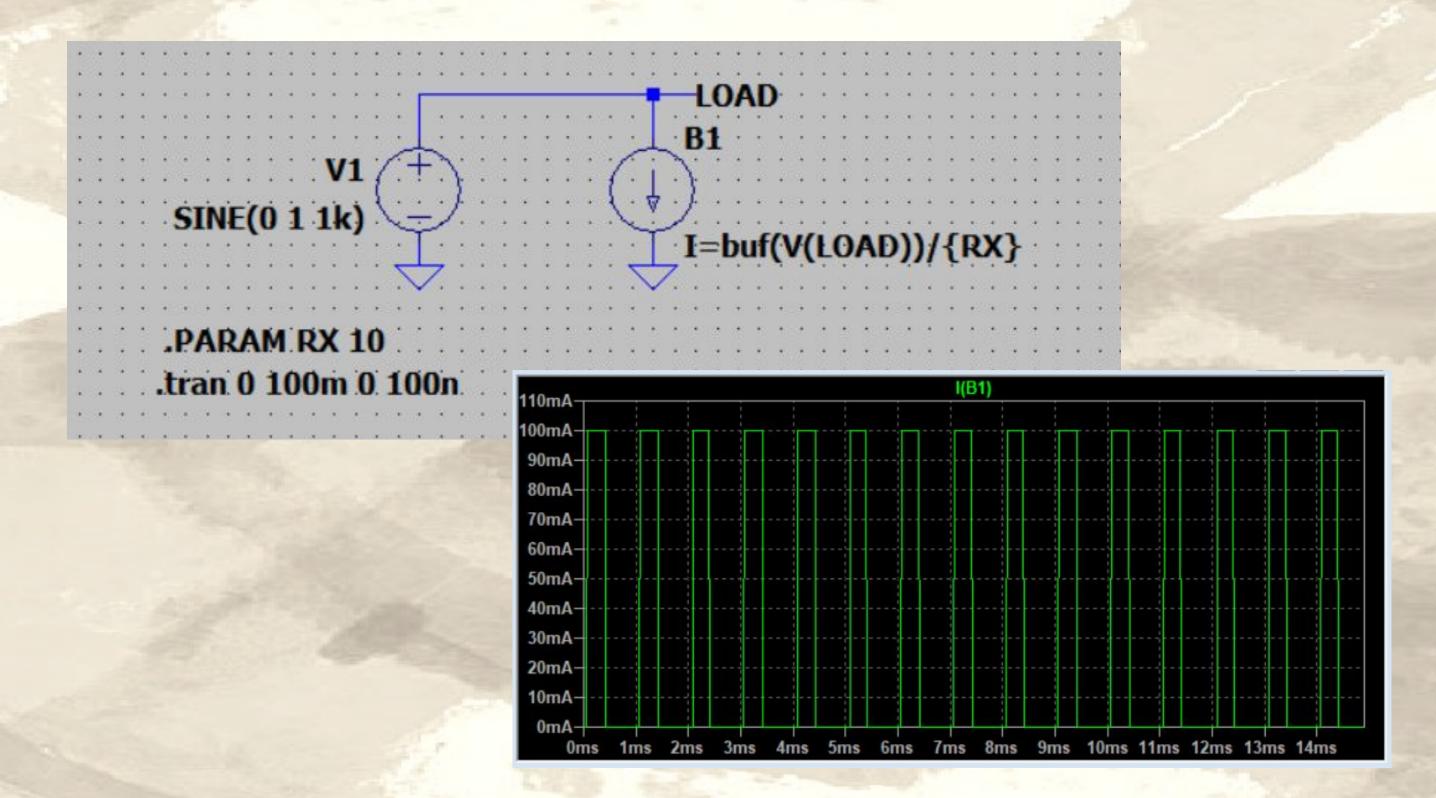It is the perfect solution for complex and non-linear loads.



Francesco Sacco linkedin.com/in/saccofrancesco